 


EE466

Nick Keister - 11443137

Lab1



\* The first line is always a comment line.

\* Case-insensitive

\* Control

.option post INGOLD=2

\* Include the following file to load transistor models.

.include './45nm\_PTM\_HP\_v2.1.pm'

\* Parameters

\* Supply voltage

.param V = 1V

\* Inverter. use NMOS\_HP and PMOS\_HP for NMOS and PMOS transistors.

\*\*\* Transistor names should begin with "m".

\*\*\* Use "nXXXXX" for node names.

\*\*\* Use 0 for the ground.

\* Format: <transistor name> <drain> <gate> <source> <body> <type> L(Length) W(Width)

mn1 n3 n2 n1 NMOS\_HP L=45n W=50n

mn2 0 n4 n3 NMOS\_HP L=45n W=50n

mn3 0 n5 n1 NMOS\_HP L=45n W=50n

mp1 nout n1 V PMOS\_HP L=45n W=75n

mn4 0 n1 nout NMOS\_HP L=45n W=50n

\*\*\* Output load capacitance. Capacitors should begin with "c".

\* Format: <capacitor name> <node 1> <node 2> <value>

cap nout 0 10f

\* Power supply

\* Format: <power supply name> <node 1> <node 2> <value>

\*\*\* Voltage source names should begin with "v".

VVdd V nout V

\* Input signal (independent voltage source)

\* Format: <signal name> <node 1> <node 2> <signal>

\* For the signal, we use a piecewise linear (PWL) source. Format: ... PWL time1 value1 time2 value2 ...

VA n2 0 PWL

+ 0 0

+ 500p 0

+ 510p 0

+ 990p 0

+ 1n 0

+ 1.5n 0

+ 1.51n V

+ 1.99n V

+ 2n 0

+ 2.5n 0

+ 2.51n V

+ 2.99n V

+ 3n 0

+ 4n 0

VB n4 0 PWL

+ 0 0

+ 500p 0

+ 510p 0

+ 990p 0

+ 1n 0

+ 1.5n 0

+ 1.51n V

+ 1.99n V

+ 2n 0

+ 2.5n 0

+ 2.51n V

+ 2.99n V

+ 3n 0

+ 4n 0

VC n5 0 PWL

+ 0 0

+ 500p 0

+ 510p V

+ 990p V

+ 1n 0

+ 1.5n 0

+ 1.51n 0

+ 1.99n 0

+ 2n 0

+ 2.5n 0

+ 2.51n V

+ 2.99n V

+ 3n 0

+ 4n 0

\* Transient analysis. Simulate up to 5ns.

.tran 1p 5n

.end